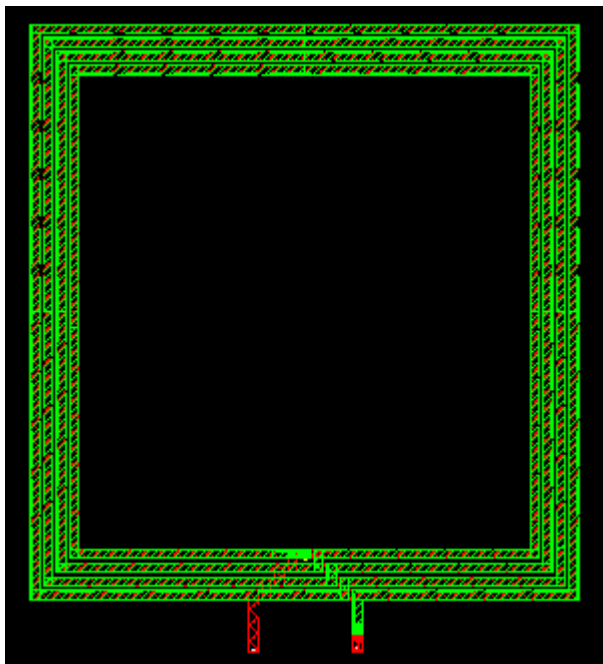




Antenna Inductance Simulation and Measurement

- Use EM Tools to simulate before layout
 - Simulate S11 and we can obtain inductance @ 13.56MHz
 - Recommendatory inductance is around 1uH ~ 2.5uH

- For Example :



ANT-135601

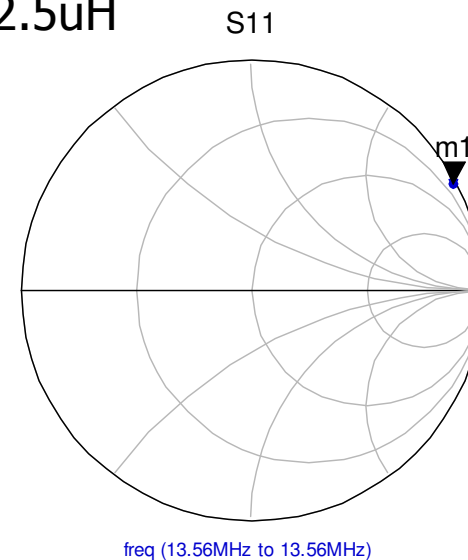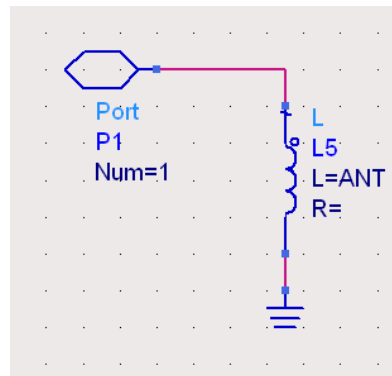


m1 freq=13.56MHz Antares_Demo_Board_S2_ANT_mom..S(1,1)=0.995 / 27.897 impedance = 2.361 + j201.283

Simulation: $2.36 + j201 \approx 1R + 2.36\mu H$

Measurement: $2.5R + 2.38\mu H$


Add Matching Circuit and Simulation

- Matching and Impedance Simulation

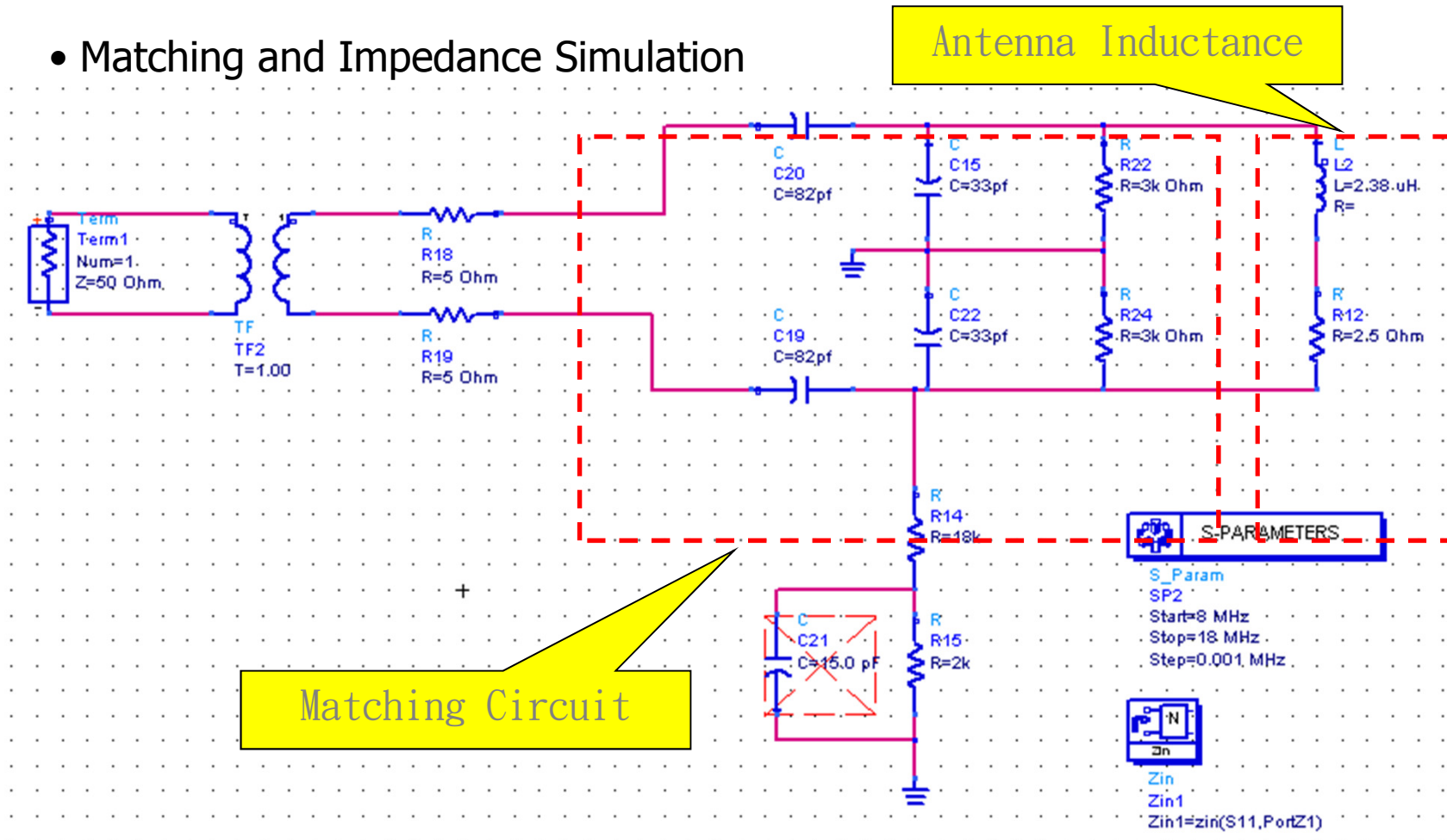


Add Matching Circuit and Simulation

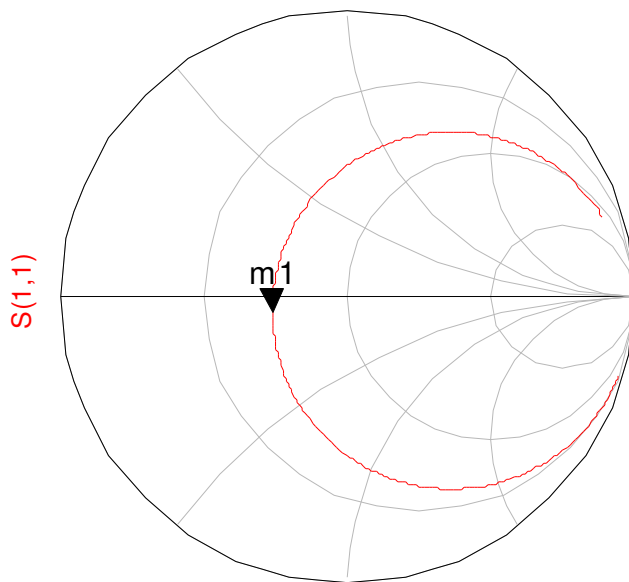- Matching and Impedance Simulation
 - Recommendatory Z_{in} is around 20 ~ 40 Ohm
 - Too small Z_{in} will cause RR10 output current more than limitation



freq (8.000MHz to 18.00MHz)

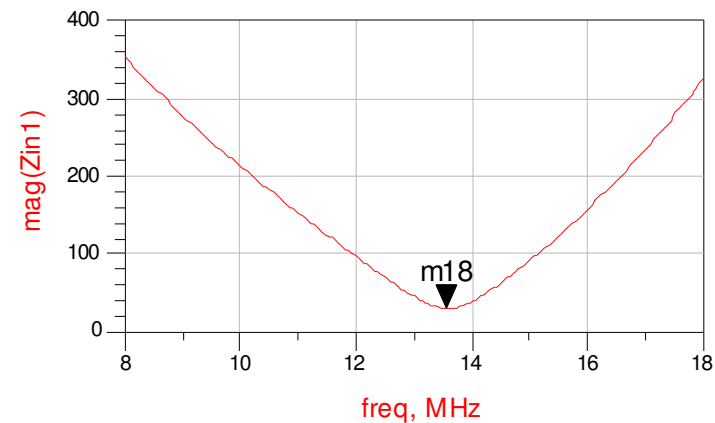
m1
freq=13.57MHz
S(1,1)=0.265 / -168.180
impedance = 29.257 - j3.416



m18
freq=13.56MHz
mag(Zin1)=29.479

Add Matching Circuit and Simulation

- Estimated Iout and BW

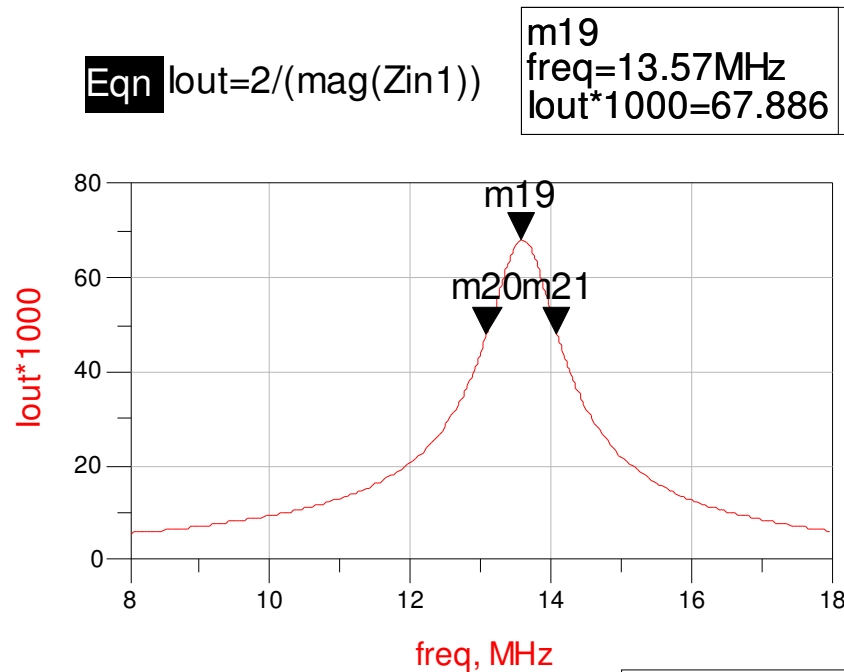

m20
freq=13.08MHz
Iout*1000=48.041

m21
freq=14.08MHz
Iout*1000=48.015

Eqn $I_{3dB} = 67.886 / 1.4142$

Eqn $BW = 14.08 - 13.08$

Eqn $QL = 13.56 / BW$


I3dB	BW	QL
48.003	1.000	13.560

$I_{out}(p-p) = 68 \text{ mA}$; $BW = 1 \text{ MHz}$; $Q = 13.5$

Measure your Matching

- HF TX and RX related circuit


TX differential matching circuits

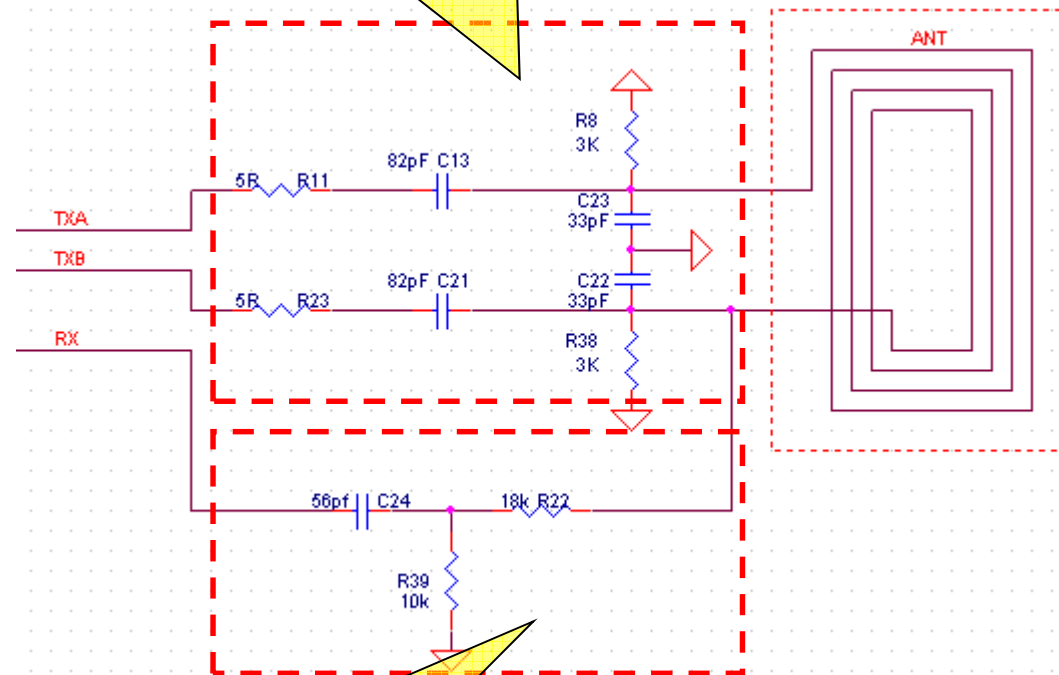

RX external circuits

Measure your Matching


- Method 1 to measure matching

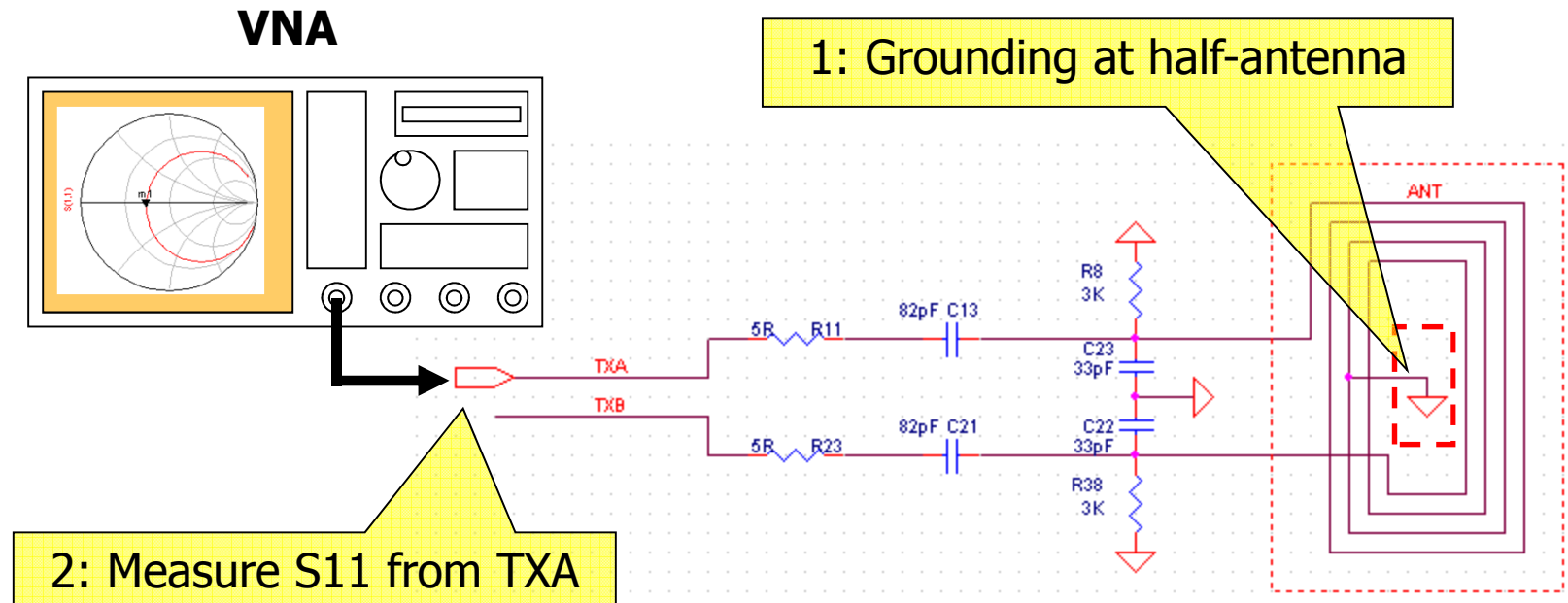

- If you matching to 30Ω, you can measure around **15 Ω** in the condition

Measure your Matching


- Method 2 to measure matching

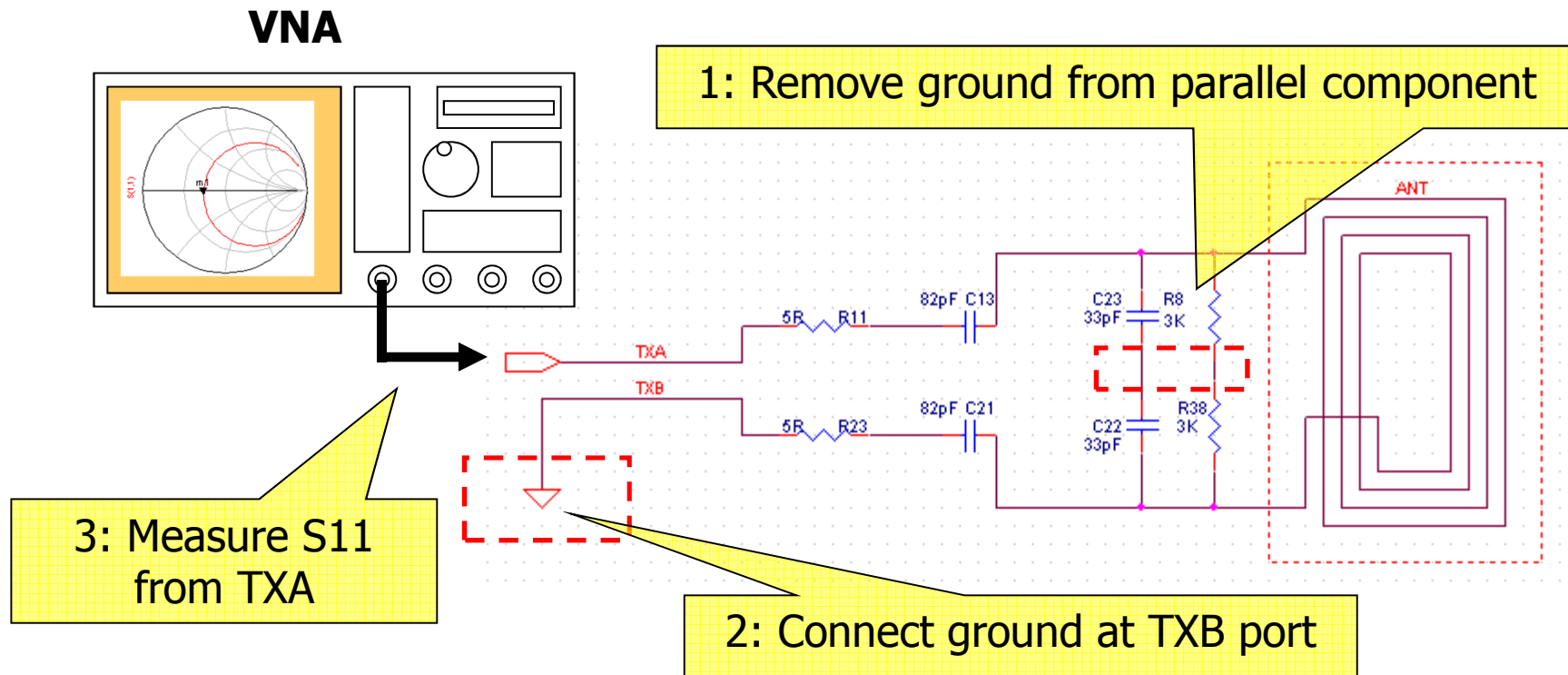

- If your matching is 30Ω, you can measure around **30 Ω** in the condition


Measure your Matching

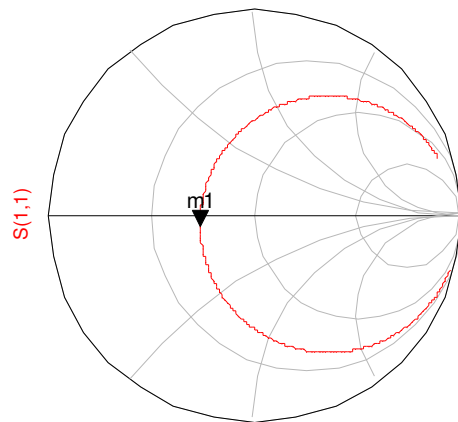- Different measure result of each method




freq (8.000MHz to 18.00MHz)

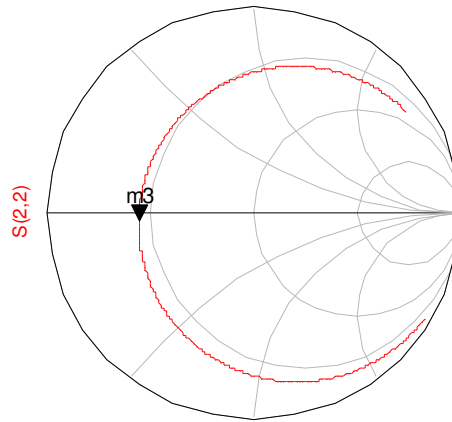m1
freq=13.56MHz
S(1,1)=0.267 / -166.220
impedance = 29.214 - j3.999




freq (8.000MHz to 18.00MHz)

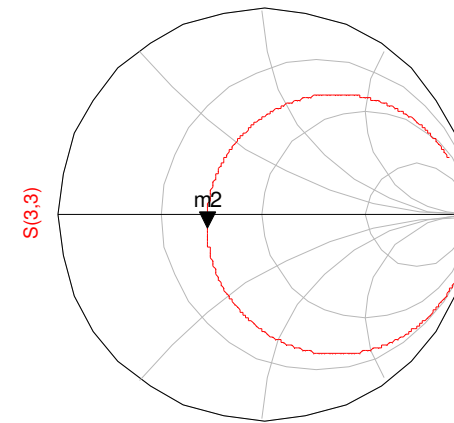m3
freq=13.56MHz
S(2,2)=0.560 / -175.323
impedance = 14.115 - j1.879



freq (8.000MHz to 18.00MHz)

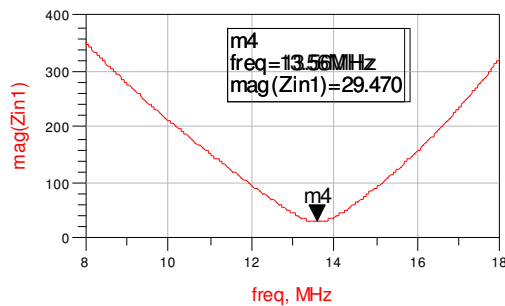
m2
freq=13.56MHz
S(3,3)=0.283 / -166.883
impedance = 28.217 - j3.934



m4
freq=13.56MHz
mag(Zin1)=29.470

freq, MHz


Simulation result

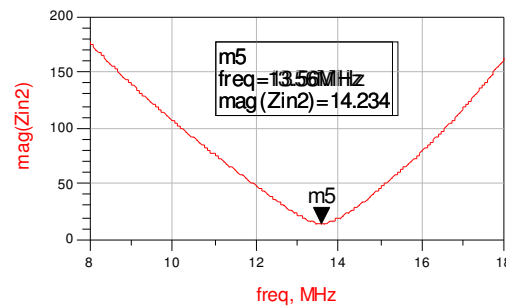

m5
freq=13.56MHz
mag(Zin2)=14.234

freq, MHz

Method 1 impedance

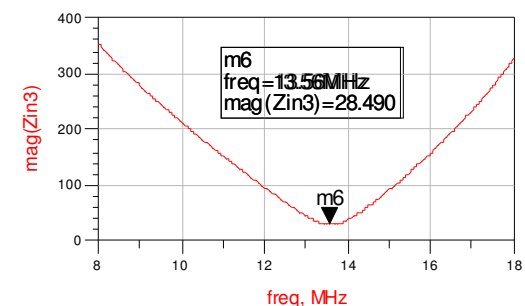


m6
freq=13.56MHz
mag(Zin3)=28.490

freq, MHz

Method 2 impedance

Measure Antenna Coil Voltage

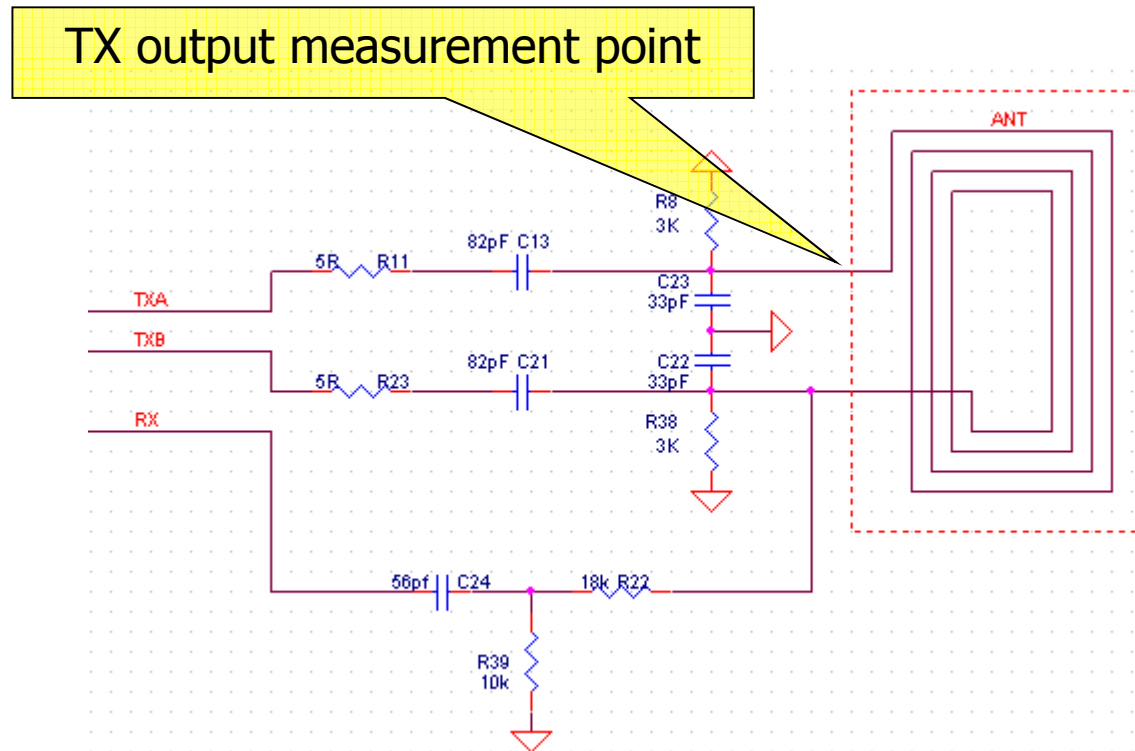- Recommendatory antenna output voltage is around 10 ~ 20 Vpp at antenna coil to ground.
- You can modify matching circuit Zin to obtain wanted output voltage.



Fine Tune Rx Input Voltage

- Recommendatory RX input voltage is around 0.8 ~ 1.5 Vpp at RX measurement point.
- You can fine tune R39 to obtain suitable voltage.

